


< 실습과제 7 >

2017253041 홍성우

1.

통합모듈 부분의 reset을 ~reset으로 바꿔 설계하는 걸 까먹어서 1번문제만 키트의 reset 신호를 누르면서 진행했습니다. 모든 문제의 핀 번호는 과제에 제시된 그대로 지정해서 사용했습니다.

(1)

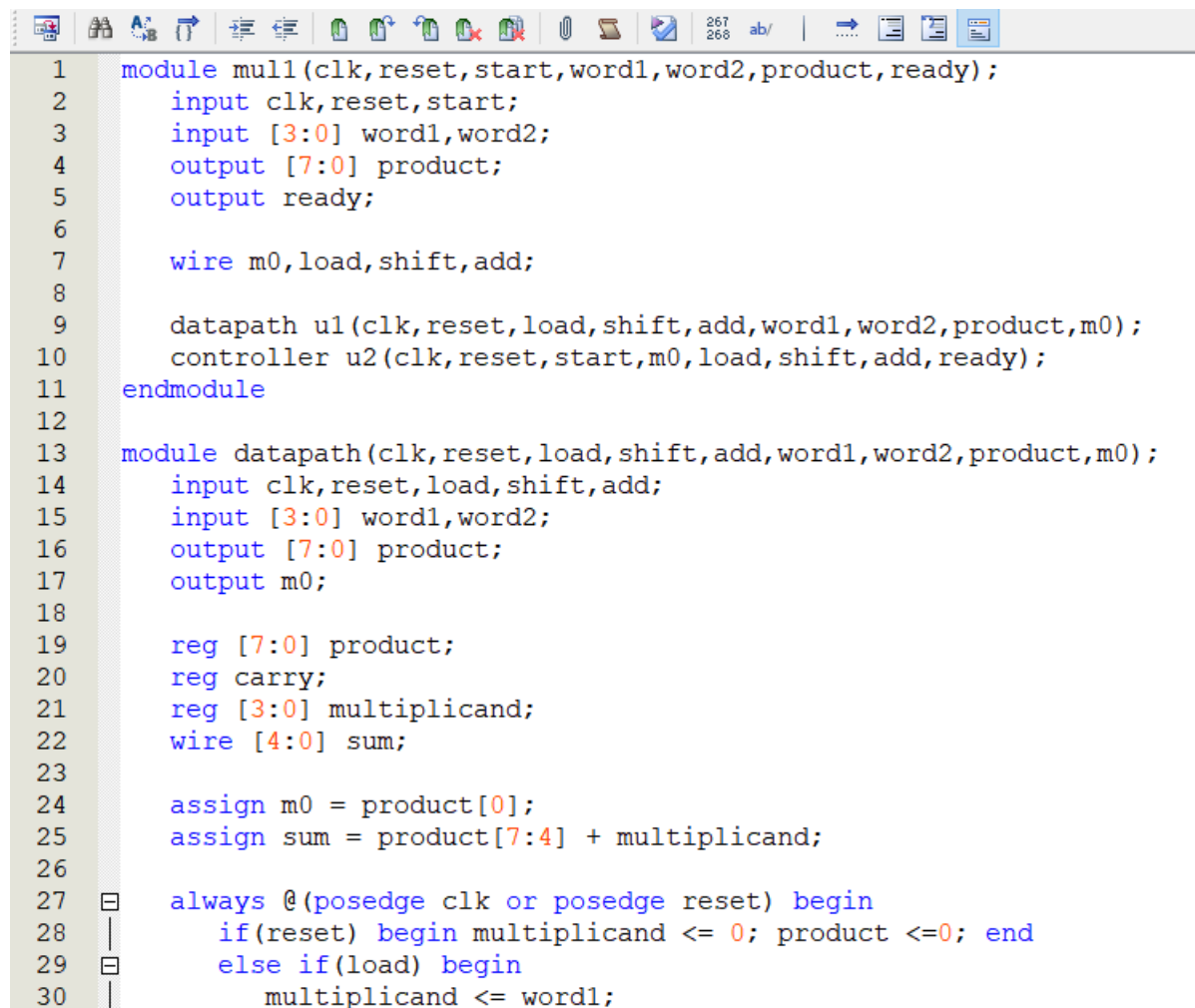


```
1  module mul1(clk,reset,start,word1,word2,product,ready);
2      input clk,reset,start;
3      input [3:0] word1,word2;
4      output [7:0] product;
5      output ready;
6
7      wire m0,load,shift,add;
8
9      datapath u1(clk,reset,load,shift,add,word1,word2,product,m0);
10     controller u2(clk,reset,start,m0,load,shift,add,ready);
11 endmodule
12
13 module datapath(clk,reset,load,shift,add,word1,word2,product,m0);
14     input clk,reset,load,shift,add;
15     input [3:0] word1,word2;
16     output [7:0] product;
17     output m0;
18
19     reg [7:0] product;
20     reg carry;
21     reg [3:0] multiplicand;
22     wire [4:0] sum;
23
24     assign m0 = product[0];
25     assign sum = product[7:4] + multiplicand;
26
27     always @(posedge clk or posedge reset) begin
28         if(reset) begin multiplicand <= 0; product <=0; end
29         else if(load) begin
30             multiplicand <= word1;
```

```


30         multiplicand <= word1;
31         product <= {4'b0,word2};|
32     end
33     else if(shift) begin
34         product <= {carry,product[7:1]}; carry <= 0;
35     end
36     else if(add) {carry,product[7:4]} <= sum;
37     end
38 endmodule
39
40 module controller(clk,reset,start,m0,load,shift,add,ready);
41     input clk,reset,start,m0;
42     output load,shift,add,ready;
43
44     reg[3:0] state;
45     localparam s0=0,s1=8,s2=9,s3=10,s4=11,s5=12,s6=13,s7=14,s8=15;
46
47     always @(posedge clk or posedge reset) begin
48         if(reset) state <= s0;
49         else
50             case(state)
51                 s0: if(start) begin state <= s1; end
52                 s1: if(m0) state <= s2; else state <= s3;
53                 s2: state <= s3;
54                 s3: if(m0) state <= s4; else state <= s5;
55                 s4: state <= s5;
56                 s5: if(m0) state <= s6; else state <= s7;
57                 s6: state <= s7;
58                 s7: if(m0) state <= s8; else state <= s0;
59                 s8: state <= s0;
60             endcase
61         end
62
63     assign load = (state==s0) && start;
64     assign shift = (state==s1||state==s3||state==s5||state==s7) && ~m0 ||
65                 (state==s2||state==s4||state==s6||state==s8);
66     assign add = (state==s1||state==s3||state==s5||state==s7) && m0;
67     assign ready = (state==s0) && ~reset;
68 endmodule
69

```


(2)

 


(3)

 

1111과 0101의 곱셈이다

 

clk 신호를 주니 shift 하는 것을 확인할 수 있다.

 

계산결과가 01001011로 올바르게 출력됐다.

2.

(1)


```
1  module mul2(clk,reset,start,word1,word2,product,ready);
2      input clk,reset,start;
3      input [3:0] word1,word2;
4      output [7:0] product;
5      output ready;
6
7      wire m0,load,shift,addshift,sub;
8
9      datapath u1(clk,~reset,load,shift,addshift,sub,word1,word2,product,m0);
10     controller u2(clk,~reset,start,m0,load,shift,addshift,sub,ready);
11 endmodule
12
13 module datapath(clk,reset,load,shift,addshift,sub,word1,word2,product,m0);
14     input clk,reset,load,shift,addshift,sub;
15     input [3:0] word1,word2;
16     output [7:0] product;
17     output m0;
18
19     reg [7:0] product;
20     reg [3:0] multiplicand;
21     wire [4:0] sum;
22     wire [4:0] eproduct,emcand;
23
24     assign m0 = product[0];
25     assign eproduct = {product[7],product[7:4]};
26     assign emcand = {multiplicand[3],multiplicand};
27     assign sum = sub ? (eproduct - emcand) : (eproduct + emcand);
28
29     always @(posedge clk or posedge reset) begin
30         if(reset) begin multiplicand <= 0; product <=0; end
```

```


30     if(reset) begin multiplicand <= 0; product <=0; end
31   else if(load) begin
32     multiplicand <= word1;
33     product <= {4'b0,word2};
34   end
35   else if(shift)
36     product <= {product[7],product[7:1]};
37   else if(addshift) product <= {sum,product[3:1]};
38   end
39 endmodule
40
41 module controller(clk,reset,start,m0,load,shift,addshift,sub,ready);
42   input clk,reset,start,m0;
43   output load,shift,addshift,sub,ready;
44
45   reg state;
46   reg [1:0] count;
47   localparam s0=0,s1=1;
48
49   always @(posedge clk, posedge reset) begin
50     if(reset) begin state <= s0; count <= 0; end
51     else
52       case(state)
53       s0: if(start) begin state <= s1; count <= 3; end
54       s1: if(count ==0) state <= s0; else count <= count - 1;
55       endcase
56   end
57
58   assign load = (state==s0) && start;
59   assign shift = (state==s1) && ~m0;
60
61   assign shift = (state==s1) && ~m0;
62   assign addshift = (state==s1) && m0;
63   assign sub = (state==s1) && (count==0);
64   assign ready = (state==s0) && ~reset;
65 endmodule
66

```


(2)

 


(3)

 

1101과 1011의 곱셈이다.

 

clk신호를 주니 addshift 하는 것을 확인할 수 있다.

 

계산결과가 00001111로 올바르게 출력됐다.